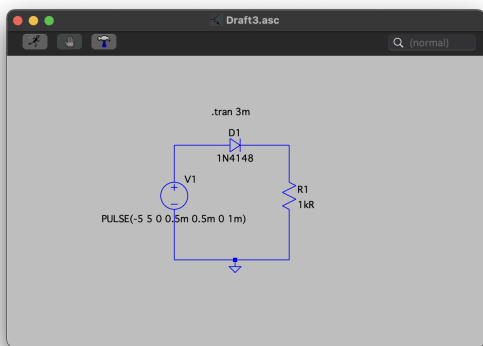


Pre-Lab 3-Diode iv Characteristics, Zener Diode, Clipper circuit

Experiment 1:

Simulation:

1)



←Figure 1

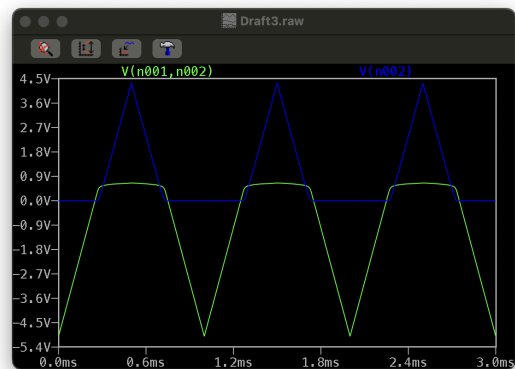


Figure 2 →

Created the schematic (**Figure1**) given in the lab into LTspice and plotted the graph (**Figure 2**)
 $V_D = V(n001, n002)$ and $V_R = V(n002)$

2)




The forward-bias region is where V_D is greater than 0, but the diode is forward-biased not until around 0.6V.

The reverse bias region would be where V_D is less than 0V.

Experiment 2:

Circuit Analysis:

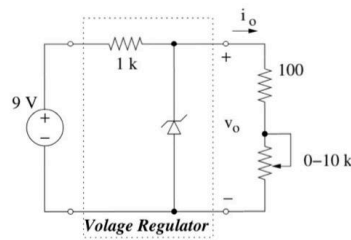

Zener Region

$V_o = -V_p = -5.6V$, but $i_o \geq 0$ so not possible

Diode on

$V_o = -V_p = -0.7V$, but $i_p \geq 0$ so not possible

Diode off

$V_o = -V_p$, $i_o = 0$, so $V_p = -i_o(1000\Omega) \Rightarrow V_o = 1000i_o$

Maximum Load Current

Zener Region

$1000i_i + 5.6V = 9V \Rightarrow 1000i_i = 3.4V \Rightarrow i_i = 3.4mA$ $i_o = \frac{5.6V}{100} = 56mA$ not possible $i_i < i_o$


Diode on

$1000i_i = 9V + 0.7V \Rightarrow 1000i_i = 9.7V \Rightarrow i_i = 9.7mA$ $i_o = \frac{-0.7V}{100} = -7mA$ not possible $i_i > i_o$

Diode off

$i_i = i_o \Rightarrow 1000i_o + 100i_o = 9V \Rightarrow i_o = 8.18mA$ $i_o = \frac{V_o}{100} \Rightarrow V_o = (8.18)(100) = 818V \Rightarrow V_o = -0.818V$ so $i_o = 8.18mA$

Simulation:

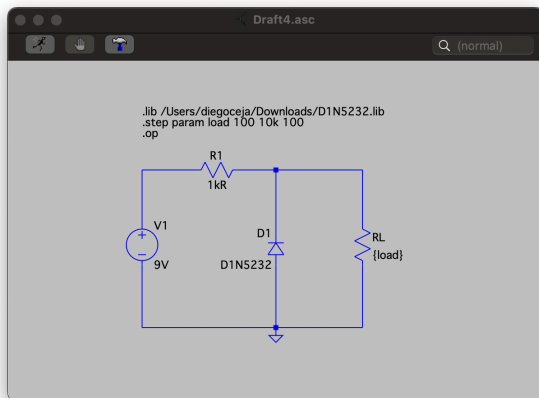

←Figure 3

Figure 4 →

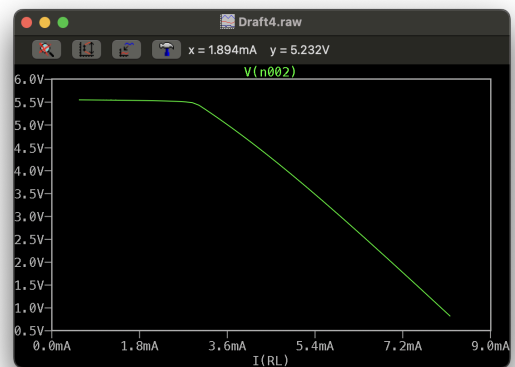


Figure 4 is where the output current is its maximum value, which is approximately 0.818V and the current through the V_1 , R_1 , and R_L , are all approximately 0.818mA, matching my results obtained through the circuit analysis.